



Memory System Organization & Architecture

Module 4

Outline

- Internal Organization of Memory Chip
- Organization of a SRAM memory unit
- Design of memory modules

Memory

- It's all about storing bits – binary digits
- Vacuum tubes, CRT, Drums, Disks and ICs
- Issues – size, cost and speed
- Semiconductor memories (Chips)


Terminology

- **Memory Access Time**: Time between read and the MFC (Memory Function Complete) signal.
- **Memory Cycle Time**: The minimum time delay required between the initiation of two successive memory operations.
- **Random Access Memory (RAM)**: Any location can be accessed for a read or write operation in some fixed amount of time that is independent of the location's address.

Semiconductor RAM Memories

- Semiconductor memories are available in a wide range of speeds.
- Their cycle time range from 100ns to less than 10ns.
- Obviously the speed of the processor depends on the speed of the memory

Internal Organization of Memory Cells

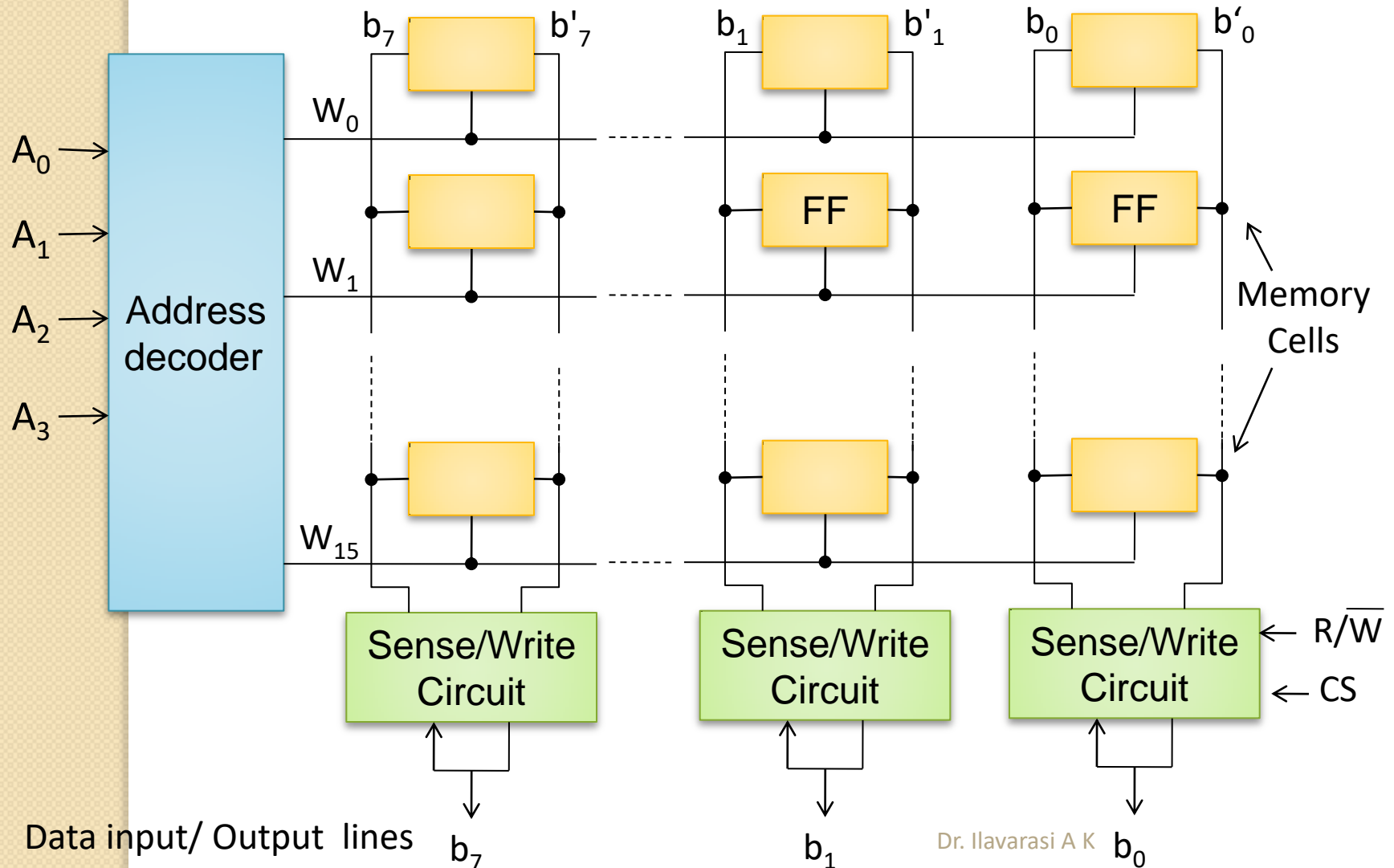


Internal Organization of Memory Cells

- Above Example: 128 bit chip
 - It has 4 address lines and 8 data lines
 - Using 4 address lines ($A_3A_2A_1A_0$) 16 word signals ($W_{15} \dots W_1 W_0$) are generated with help of decoder 4:16 decoder
 - 16 words of each 8 bits ($= 16 \times 8 \text{ bits} = 128 \text{ bits}$)
 - For any given input address lines ($A_3A_2A_1A_0$) only one of the word lines from $W_{15} \dots W_0$ will be active at a time.
 - Which in turn enable the complete row of the memory cells connected to W_i bit
 - Using R/**W** and CS signal one can enable the Sense/Write Circuits of the all bits ranging from b_7 to b_0

Chip with 1024 Memory Cells

 
- 1024 bits can be planned as 128 x 8 memory
- Total address lines required $128 = 2^N \rightarrow N = \log_2 128 = 7$, it means it should have $A_6 \dots A_1 A_0$
- It means 128 x 8 bits (Similar to 16 x 8 bits)




8 Data Lines

Chip with 1024 Memory Cells


- Or it could be 1024 x 1

 

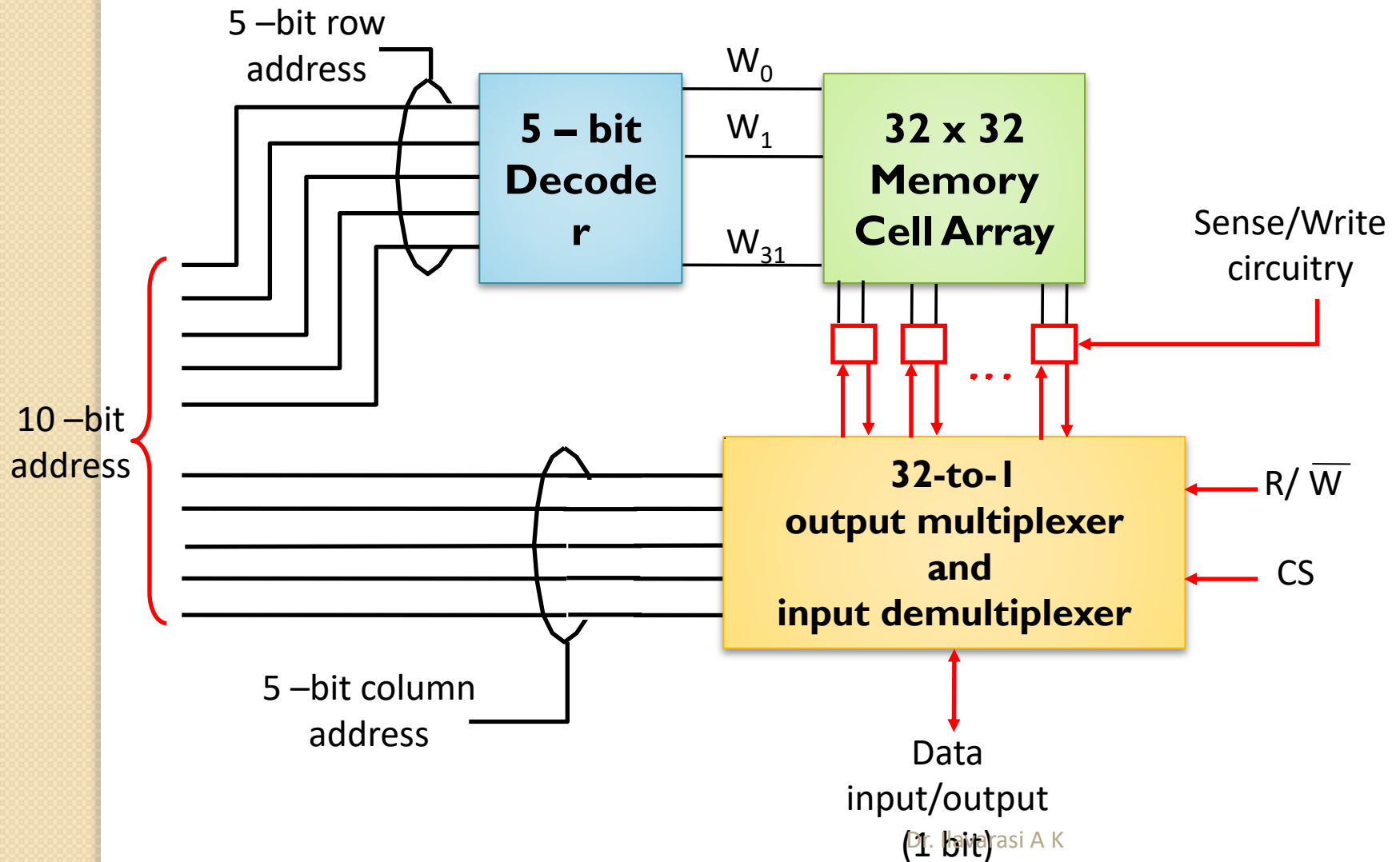Organization of a $1K \times 1$ memory chip




Larger Memories Using Multiple Chips

 

512K x 8 Memory Chip


- Organization of a 2M x 32 memory module using 512K x 8 static memory chips
- $2\text{M} \times 32 \rightarrow 2 \times 2^{10} \times 2^{10} \times 32 \rightarrow 2^{21} \times 32$
- No. of 512K x 8 required = $(2^{21} \times 32) / (2^9 \times 2^{10} \times 8) = 16$ nos.

Larger Memories Using Multiple Chips

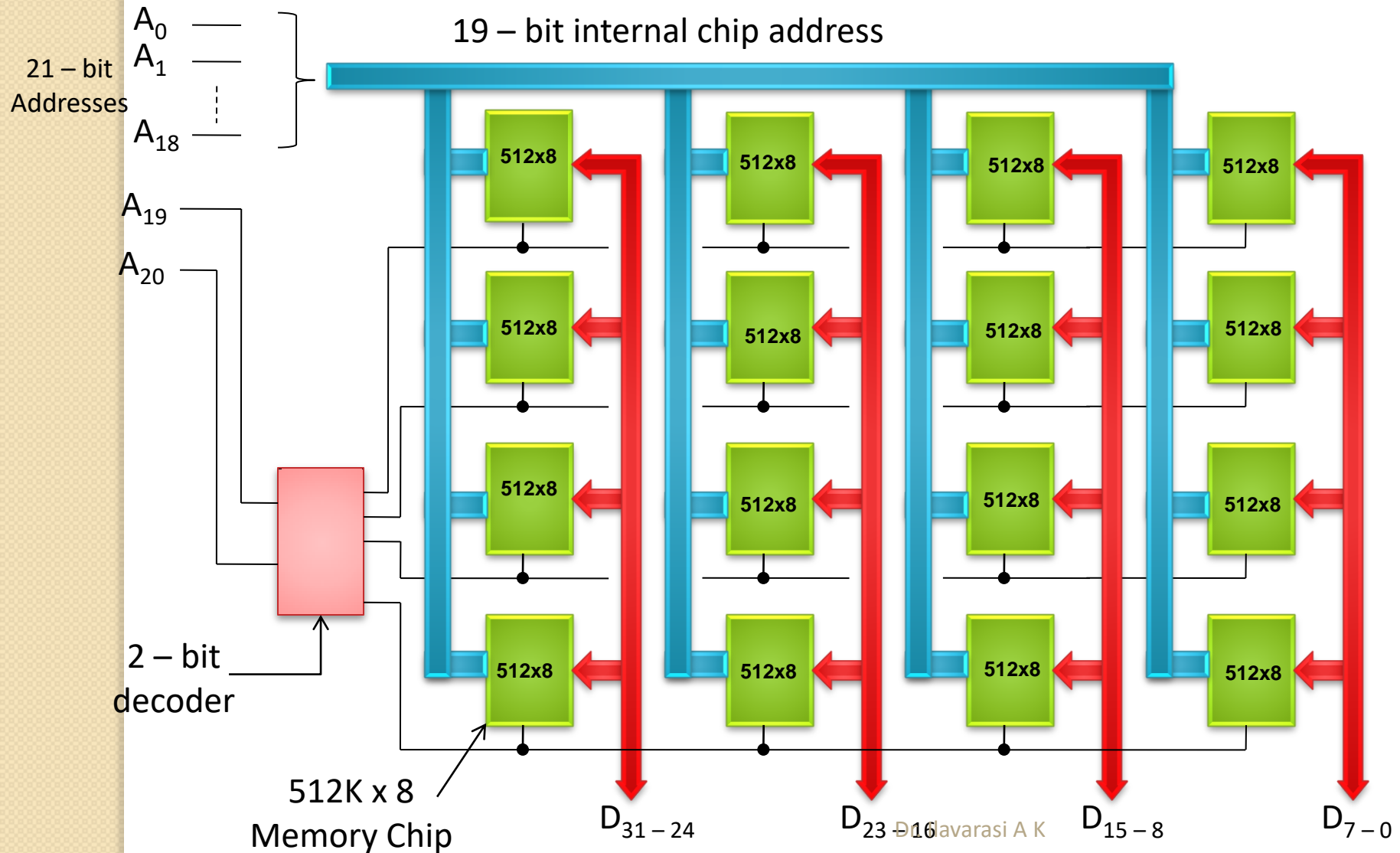

Larger Memories Using Multiple Chips

 - Assembly of several memory chips on a separate small board (PCB) that plugs vertically into a single socket on the motherboard called as Memory Modules
 - SIMMs – Single In-line Memory Modules
 - DIMMs – Dual In-line Memory Modules



Memory System Considerations

- The choice of a RAM chip for a given application depends on several factors
 - Cost,
 - Speed
 - Power dissipation and
 - Size of the chip
- Static RAMs are generally used only when very fast operation is the primary requirement
 - They are used mostly in cache memories
- Dynamic RAMs are the predominant choice for implementing computer main memories